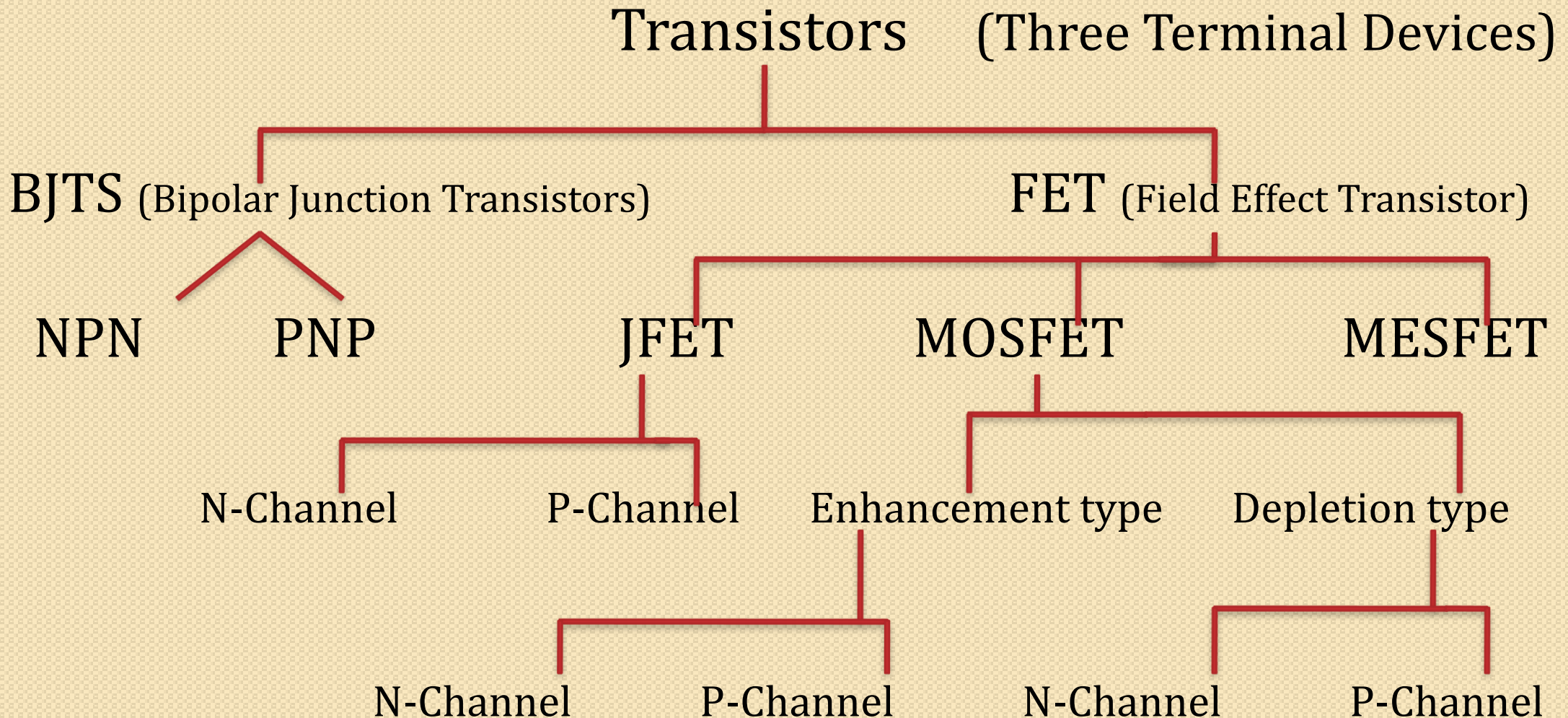


# UNIT-4

# MOS FIELD-EFFECT TRANSISTORS ( MOSFETS)




# Introduction



# Comparison Between BJTs & FETs


## BJTs

I. Current Controlled Device

 

## FETs

Voltage Controlled device

 

2. Bipolar device

Unipolar device

3. Has low I/P impedance

Has high I/P impedance

4. Occupies more space

Occupies less space

5. Stability against temperature is less

More temperature stable than BJT

6. AC voltage gains for BJT amplifier is more

AC voltage gain for FET amplifier is less

7. Highly susceptible to more noise.

Less susceptible to less noise.

8.  $I_C = \beta I_B$

$$I_D = I_{Dss} (1 - V_{GS}/V_p)$$

$$I_C = I_E$$

$$I_D = I_S$$

$V_{BE} = 0.7V$   
(starting point for analysis)

$I_G = 0A$   
(starting point for analysis)


9. Power dissipation is more.

Power dissipation is less.

10. Used in amplifiers, switches, digital logic & memory.


Used in amplifiers, switches, filters, memory, digital logic ICs such as microprocessor, microcontrollers, signal processors, etc.

**FIG 4.1 SHOWS THE PHYSICAL STRUCTURE OF ENHANCEMENT TYPE NMOS TRANSISTOR ; PERSPECTIVE VIEW. TYPICALLY  $L=0.1$  TO  $3\mu m$ ,  $W=0.2$  TO  $100\mu m$ , AND THE THICKNESS OF THE OXIDE LAYER ( $t_{ox}$ ) IS IN THE RANGE OF 2 TO 50 nm.**

 


 
## FIG 4.1 (B) PHYSICAL STRUCTURE OF ENHANCEMENT TYPE NMOS TRANSISTOR----- CROSS SECTIONAL VIEW.



Another name for the MOSFET is the insulated-gate FET or IGFET.



# MOS FET FEATURES

- L is in the range of  $0.1\text{ }\mu\text{m}$  to  $3\text{ }\mu\text{m}$ , and
- W is in the range of  $0.2\text{ }\mu\text{m}$  to  $100\mu\text{m}$ .
- note that the MOSFET is a symmetrical device; thus its
- source and drain can be interchanged with no change in device characteristics
- Operation with No Gate Voltage
- These back -to-back diodes prevent current conduction from drain to source when a voltage  $V_{DS}$  is applied
- In fact, the path between drain and
- source has a very high resistance (of the order of  $10^{12}\text{ }\Omega$ ).



FIG 4.2 SHOWS THE ENHANCEMENT TYPE NMOS TRANSISTOR WITH A POSITIVE VOLTAGE APPLIED TO THE GATE. AN N CHANNEL IS INDUCED AT THE TOP OF THE SUBSTRATE BENEATH THE GATE.


 


FIG 4.3 SHOWS AN NMOS TRANSISTOR WITH  $V_{GS} > V_t$  AND WITH A SMALL  $V_{DS}$  APPLIED. THE DEVICE ACTS AS A RESISTANCE WHOSE VALUE IS DETERMINED BY  $V_{GS}$ .

 

## FIG 4.4 SHOWS THE $I_D$ - $V_{DS}$ CHARACTERISTICS OF THE MOSFET.

 




FIG 4.5 SHOWS THE OPERATION OF THE ENHANCEMENT NMOS TRANSISTOR AS  $V_{DS}$  IS INCREASED. THE INDUCED CHANNEL ACQUIRES A TAPERED SHAPE, AND ITS RESISTANCE INCREASES AS  $V_{DS}$  IS INCREASED. HERE  $V_{GS}$  IS KEPT CONSTANT AT VALUE  $> V_t$

 


FIG 4.6 SHOWS THE DRAIN CURRENT  $I_D$  VERSUS THE DRAIN-TO-SOURCE VOLTAGE  $V_{DS}$  FOR AN ENHANCEMENT-TYPE NMOS TRANSISTOR OPERATED WITH  $V_{GS} > V_t$ .



 


FIG 4.7 SHOWS INCREASING  $V_{DS}$  CAUSES THE CHANNEL TO ACQUIRE A TAPERED SHAPE. EVENTUALLY, AS  $V_{DS}$  REACHES  $V_{GS} - V_t$ , THE CHANNEL IS PINCHED OFF AT THE DRAIN END. INCREASING  $V_{DS} - V_t$  HAS LITTLE EFFECT (THEORETICALLY, NO EFFECT) ON THE CHANNEL'S SHAPE.

 

 

**FIG 4.8 SHOWS THE DERIVATION OF THE  $I_D$ - $V_{DS}$  CHARACTERISTICS OF THE NMOS TRANSISTOR.**



The reader will recall that in the MOSFET, the gate and the channel region form a parallel-plate capacitor for which the oxide layer serves as a dielectric. If the capacitance per unit gate area is denoted  $C_{ox}$  and the thickness of the oxide layer is  $t_{ox}$ , then

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \quad (4.2)$$

where  $\epsilon_{ox}$  is the permittivity of the silicon oxide,

$$\epsilon_{ox} = 3.9\epsilon_0 = 3.9 \times 8.854 \times 10^{-12} = 3.45 \times 10^{-11} \text{ F/m}$$

The oxide thickness  $t_{ox}$  is determined by the process technology used to fabricate the MOSFET. As an example, for  $t_{ox} = 10 \text{ nm}$ ,  $C_{ox} = 3.45 \times 10^{-3} \text{ F/m}^2$ , or  $3.45 \text{ fF}/\mu\text{m}^2$  as it is usually expressed.

Now refer to Fig. 4.8 and consider the infinitesimal strip of the gate at distance  $x$  from the source. The capacitance of this strip is  $C_{ox}W dx$ . To find the charge stored on this infinitesimal strip of the gate capacitance, we multiply the capacitance by the *effective voltage*

between the gate and the channel at point  $x$ , where the effective voltage is the voltage that is responsible for inducing the channel at point  $x$  and is thus  $[v_{GS} - v(x) - V_t]$  where  $v(x)$  is the voltage in the channel at point  $x$ . It follows that the electron charge  $dq$  in the infinitesimal portion of the channel at point  $x$  is

$$dq = -C_{ox}(W dx)[v_{GS} - v(x) - V_t] \quad (4.3)$$

where the leading negative sign accounts for the fact that  $dq$  is a negative charge.

The voltage  $v_{DS}$  produces an electric field along the channel in the negative  $x$  direction. At point  $x$  this field can be expressed as

$$E(x) = -\frac{dv(x)}{dx}$$

The electric field  $E(x)$  causes the electron charge  $dq$  to *drift* toward the drain with a velocity  $dx/dt$ ,

$$\frac{dx}{dt} = -\mu_n E(x) = \mu_n \frac{dv(x)}{dx} \quad (4.4)$$

where  $\mu_n$  is the mobility of electrons in the channel (called surface mobility). It is a physical parameter whose value depends on the fabrication process technology. The resulting drift current  $i$  can be obtained as follows:

$$\begin{aligned} i &= \frac{dq}{dt} \\ &= \frac{dq}{dx} \frac{dx}{dt} \end{aligned}$$

Substituting for the charge-per-unit-length  $dq/dx$  from Eq. (4.3), and for the electron drift velocity  $dx/dt$  from Eq. (4.4), results in

$$i = -\mu_n C_{ox} W [v_{GS} - v(x) - V_t] \frac{dv(x)}{dx}$$

Although evaluated at a particular point in the channel, the current  $i$  must be constant at all points along the channel. Thus  $i$  must be equal to the source-to-drain current. Since we are interested in the drain-to-source current  $i_D$ , we can find it as

$$i_D = -i = \mu_n C_{ox} W [v_{GS} - v(x) - V_t] \frac{dv(x)}{dx}$$

where  $\mu_n$  is the mobility of electrons in the channel (called surface mobility). It is a physical parameter whose value depends on the fabrication process technology. The resulting drift current  $i$  can be obtained as follows:

$$\begin{aligned} i &= \frac{dq}{dt} \\ &= \frac{dq}{dx} \frac{dx}{dt} \end{aligned}$$

Substituting for the charge-per-unit-length  $dq/dx$  from Eq. (4.3), and for the electron drift velocity  $dx/dt$  from Eq. (4.4), results in

$$i = -\mu_n C_{ox} W [v_{GS} - v(x) - V_t] \frac{dv(x)}{dx}$$

Although evaluated at a particular point in the channel, the current  $i$  must be constant at all points along the channel. Thus  $i$  must be equal to the source-to-drain current. Since we are interested in the drain-to-source current  $i_D$ , we can find it as

$$i_D = -i = \mu_n C_{ox} W [v_{GS} - v(x) - V_t] \frac{dv(x)}{dx}$$



Integrating both sides of this equation from  $x = 0$  to  $x = L$  and, correspondingly, for  $v(0) = 0$  to  $v(L) = v_{DS}$ ,

$$\int_0^L i_D dx = \int_0^{v_{DS}} \mu_n C_{ox} W [v_{GS} - V_t - v(x)] dv(x)$$

gives

$$i_D = (\mu_n C_{ox}) \left( \frac{W}{L} \right) \left[ (v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

This is the expression for the  $i_D$ - $v_{DS}$  characteristic in the triode region. The value of the current at the edge of the triode region or, equivalently, at the beginning of the saturation region can be obtained by substituting  $v_{DS} = v_{GS} - V_t$ , resulting in

$$i_D = \frac{1}{2} (\mu_n C_{ox}) \left( \frac{W}{L} \right) (v_{GS} - V_t)^2 \quad (4.6)$$

This is the expression for the  $i_D$ - $v_{DS}$  characteristic in the saturation region; it simply gives the saturation value of  $i_D$  corresponding to the given  $v_{GS}$ . (Recall that in saturation  $i_D$  remains constant for a given  $v_{GS}$  as  $v_{DS}$  is varied.)

In the expressions in Eqs. (4.5) and (4.6),  $\mu_n C_{ox}$  is a constant determined by the process technology used to fabricate the  $n$ -channel MOSFET. It is known as the **process transconductance parameter**, for as we shall see shortly, it determines the value of the MOSFET transconductance, is denoted  $k'$ , and has the dimensions of  $A/V^2$ .

In the expressions in Eqs. (4.5) and (4.6),  $\mu_n C_{ox}$  is a constant determined by the process technology used to fabricate the  $n$ -channel MOSFET. It is known as the **process transconductance parameter**, for as we shall see shortly, it determines the value of the MOSFET transconductance, is denoted  $k'_n$ , and has the dimensions of  $A/V^2$ :

$$k'_n = \mu_n C_{ox} \quad (4.7)$$

Of course, the  $i_D$ - $v_{DS}$  expressions in Eqs. (4.5) and (4.6) can be written in terms of  $k'_n$  as follows:

$$i_D = k'_n \frac{W}{L} \left[ (v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \quad (\text{Triode region}) \quad (4.5a)$$

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 \quad (\text{Saturation region}) \quad (4.6a)$$

In this book we will use the forms with  $(\mu_n C_{ox})$  and with  $k'_n$  interchangeably.

From Eqs. (4.5) and (4.6) we see that the drain current is proportional to the ratio of the channel width  $W$  to the channel length  $L$ , known as the **aspect ratio** of the MOSFET. The



Consider a process technology for which  $L_{\min} = 0.4 \mu\text{m}$ ,  $t_{ox} = 8 \text{ nm}$ ,  $\mu_n = 450 \text{ cm}^2/\text{V}\cdot\text{s}$ , and  $V_t = 0.7 \text{ V}$ .

(a) Find  $C_{ox}$  and  $k'_n$ .

(b) For a MOSFET with  $W/L = 8 \mu\text{m}/0.8 \mu\text{m}$ , calculate the values of  $V_{GS}$  and  $V_{DS\min}$  needed to operate the transistor in the saturation region with a dc current  $I_D = 100 \mu\text{A}$ .

(c) For the device in (b), find the value of  $V_{GS}$  required to cause the device to operate as a  $1000\text{-}\Omega$  resistor for very small  $v_{DS}$ .

$$\begin{aligned}
 \text{(a)} \quad C_{ox} &= \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11}}{8 \times 10^{-9}} = 4.32 \times 10^{-3} \text{ F/m}^2 \\
 &= 4.32 \text{ fF}/\mu\text{m}^2 \\
 k'_n &= \mu_n C_{ox} = 450 (\text{cm}^2/\text{V}\cdot\text{s}) \times 4.32 (\text{fF}/\mu\text{m}^2) \\
 &= 450 \times 10^8 (\mu\text{m}^2/\text{V}\cdot\text{s}) \times 4.32 \times 10^{-15} (\text{F}/\mu\text{m}^2) \\
 &= 194 \times 10^{-6} (\text{F}/\text{V}\cdot\text{s}) \\
 &= 194 \mu\text{A}/\text{V}^2
 \end{aligned}$$

(b) For operation in the saturation region,

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2$$

Thus,

$$100 = \frac{1}{2} \times 194 \times \frac{8}{0.8} (V_{GS} - 0.7)^2$$

$$V_{GS} - 0.7 = 0.32 \text{ V}$$

or

$$V_{GS} = 1.02 \text{ V}$$

and

$$V_{DS\min} = V_{GS} - V_t = 0.32 \text{ V}$$

(c) For the MOSFET in the triode region with  $v_{DS}$  very small,

$$i_D \cong k'_n \frac{W}{L} (v_{GS} - V_t) v_{DS}$$

from which the drain-to-source resistance  $r_{DS}$  can be found as

$$\begin{aligned} r_{DS} &\equiv \left. \frac{v_{DS}}{i_D} \right|_{\text{small } v_{DS}} \\ &= 1 / \left[ k'_n \frac{W}{L} (V_{GS} - V_t) \right] \end{aligned}$$

Thus

$$1000 = \frac{1}{194 \times 10^{-6} \times 10(V_{GS} - 0.7)}$$

which yields

$$V_{GS} - 0.7 = 0.52 \text{ V}$$

Thus,

$$V_{GS} = 1.22 \text{ V}$$



FIG 4.9 SHOWS THE CROSS SECTION OF A CMOS INTEGRATED CIRCUIT. NOTE THAT THE PMOS TRANSISTOR IS FORMED IN A SEPERATE  $n$ -TYPE REGION, KNOWN AS AN  $n$ -WELL. ANOTHER ARRANGEMENT IS ALSO POSSIBLE IN WHICH AN  $n$ -TYPE BODY IS USED AND THE N DEVICE IS FORMED IN A  $p$ -WELL.


 


FIG4.10 (A) SHOWS THE CIRCUIT SYMBOL FOR THE  $n$ -CHANNEL ENHANCEMENT-TYPE MOSFET. FIG(B) SHOWS THE MODIFIED CIRCUIT SYMBOL WITH AN ARROWHEAD ON THE SOURCE TERMINAL TO DISTINGUISH IT FROM THE DRAIN AND TO INDICATE DEVICE POLARITY ( $n$ -CHANNEL). FIG(C) SHOWS THE SIMPLIFIED CIRCUIT SYMBOL TO BE USED WHEN THE SOURCE IS CONNECTED TO THE BODY OR WHEN THE EFFECT OF THE BODY ON DEVICE OPERATION IS UNIMPORANT.

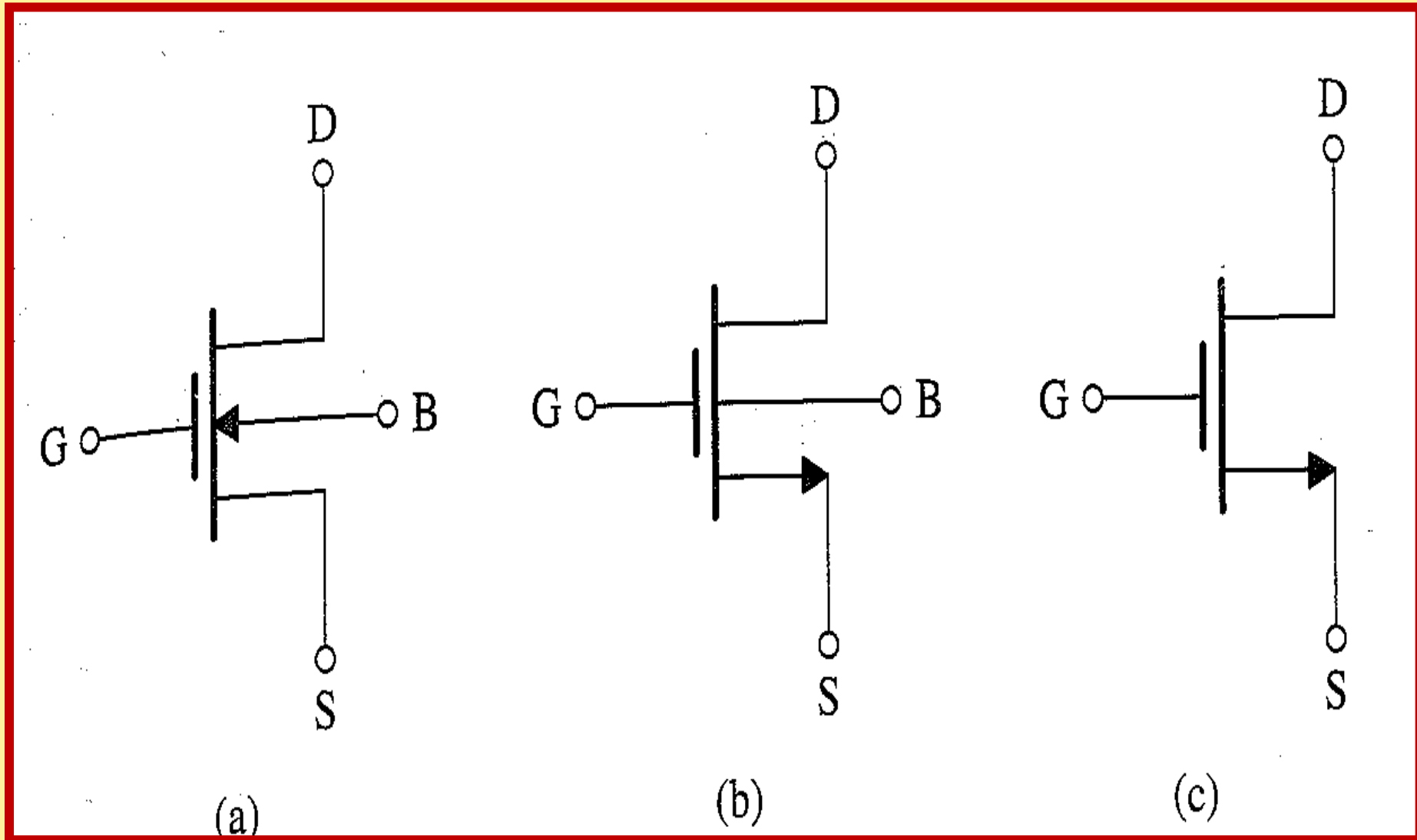


## OPERATING THE MOS TRANSISTOR IN THE SUBTHRESHOLD REGION

 - n-channel MOSFET, for  $V_{GS} < V_t$ , no current flows and the device is cut off.
- been found that for values of  $V_{GS}$  smaller than but close to  $V_t$ , a small drain current flows.
- In this subthreshold region of operation the drain current is exponentially related to  $V_{GS}$
- there are special, but a growing number of, applications that make use of subthreshold operation

 




FIG 4.11 (A) SHOWS AN  $n$ -CHANNEL ENHANCEMENT-TYPE MOSFET WITH  $V_{GS}$  AND  $V_{DS}$  APPLIED AND WITH THE NORMAL DIRECTIONS OF CURRENT FLOW INDICATED. FIG (B) SHOWS THE  $I_D$ - $V_{DS}$  CHARACTERISTICS FOR A DEVICE WITH  $K'_n(W/L)=1.0 \text{ mA/V}^2$ .



(a)



(b)



The characteristic curves in Fig. 4.11(b) indicate that there are three distinct regions of operation: the **cutoff region**, the **triode region**, and the **saturation region**. The saturation region is used if the FET is to operate as an amplifier. For operation as a switch, the cutoff and triode regions are utilized. The device is cut off when  $v_{GS} < V_t$ . To operate the MOSFET in the triode region we must first induce a channel,

$$v_{GS} \geq V_t \quad (\text{Induced channel}) \quad (4.8)$$

and then keep  $v_{DS}$  small enough so that the channel remains continuous. This is achieved by ensuring that the gate-to-drain voltage is

$$v_{GD} > V_t \quad (\text{Continuous channel}) \quad (4.9)$$

This condition can be stated explicitly in terms of  $v_{DS}$  by writing  $v_{GD} = v_{GS} + v_{SD} = v_{GS} - v_{DS}$ ; thus,

$$v_{GS} - v_{DS} > V_t$$

which can be rearranged to yield

$$v_{DS} < v_{GS} - V_t \quad (\text{Continuous channel}) \quad (4.10)$$

Either Eq. (4.9) or Eq. (4.10) can be used to ascertain triode-region operation. In words, *the n-channel enhancement-type MOSFET operates in the triode region when  $v_{GS}$  is greater than  $V_t$  and the drain voltage is lower than the gate voltage by at least  $V_t$  volts.*

In the triode region, the  $i_D$ - $v_{DS}$  characteristics can be described by the relationship of Eq. (4.5), which we repeat here,

$$i_D = k'_n \frac{W}{L} \left[ (v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \quad (4.11)$$

where  $k'_n = \mu_n C_{ox}$  is the process transconductance parameter; its value is determined by the fabrication technology. If  $v_{DS}$  is sufficiently small so that we can neglect the  $v_{DS}^2$  term in Eq. (4.11), we obtain for the  $i_D$ - $v_{DS}$  characteristics near the origin the relationship

$$i_D \simeq k'_n \frac{W}{L} (v_{GS} - V_t) v_{DS} \quad (4.12)$$

This linear relationship represents the operation of the MOS transistor as a linear resistance  $r_{DS}$  whose value is controlled by  $v_{GS}$ . Specifically, for  $v_{GS}$  set to a value  $V_{GS}$ ,  $r_{DS}$  is given by

$$r_{DS} \equiv \left. \frac{v_{DS}}{i_D} \right|_{\substack{v_{DS} \text{ small} \\ v_{GS} = V_{GS}}} = \left[ k'_n \frac{W}{L} (V_{GS} - V_t) \right]^{-1} \quad (4.13)$$

We discussed this region of operation in the previous section (refer to Fig. 4.4). It is also useful to express  $r_{DS}$  in terms of the **gate-to-source overdrive voltage**,

$$V_{OV} \equiv V_{GS} - V_t$$

as

$$r_{DS} = 1 / \left[ k'_n \left( \frac{W}{L} \right) V_{OV} \right] \quad (4.14)$$

Finally, we urge the reader to show that the approximation involved in writing Eq. (4.12) is based on the assumption that  $v_{DS} \ll 2V_{OV}$ .

To operate the MOSFET in the saturation region, a channel must be induced,

$$v_{GS} \geq V_t \quad (\text{Induced channel}) \quad (4.15)$$


and pinched off at the drain end by raising  $v_{DS}$  to a value that results in the gate-to-drain voltage falling below  $V_t$ ,

$$v_{GD} \leq V_t \quad (\text{Pinched-off channel}) \quad (4.16)$$


This condition can be expressed explicitly in terms of  $v_{DS}$  as

$$v_{DS} \geq v_{GS} - V_t \quad (\text{Pinched-off channel}) \quad (4.17)$$


**FIG 4.12 THE  $I_D$ - $V_{GS}$  CHARACTERISTICS FOR AN ENHANCEMENT-TYPE NMOS TRANSISTOR IN SATURATION ( $V_t=1V$ ,  $k'_N W/L=1.0mA/V^2$ )**

 

**FIG 4.13 SHOWS THE LARGE SIGNAL EQUIVALENT – CIRCUIT MODEL OF AN  $n$ -CHANNEL MOSFET OPERATING IN THE SATURATION REGION.**

 


**FIG 4.14 SHOWS THE RELATIVE LEVELS OF THE TERMINAL VOLTAGES OF THE ENHANCEMENT NMOS TRANSISTOR FOR OPERATION IN THE TRIODE REGION AND IN THE SATURATION REGION.**

 



# FINITE OUTPUT RESISTANCE IN SATURATION

 

**FIGURE 4.15** Increasing  $v_{DS}$  beyond  $v_{DSsat}$  causes the channel pinch-off point to move slightly away from the drain, thus reducing the effective channel length (by  $\Delta L$ ).

To account for the dependence of  $i_D$  on  $v_{DS}$  in saturation, we replace  $L$  in Eq. (4.20) with  $L - \Delta L$  to obtain

$$\begin{aligned} i_D &= \frac{1}{2} k'_n \frac{W}{L - \Delta L} (v_{GS} - V_t)^2 \\ &= \frac{1}{2} k'_n \frac{W}{L} \frac{1}{1 - (\Delta L/L)} (v_{GS} - V_t)^2 \\ &\cong \frac{1}{2} k'_n \frac{W}{L} \left( 1 + \frac{\Delta L}{L} \right) (v_{GS} - V_t)^2 \end{aligned}$$

where we have assumed that  $(\Delta L/L) \ll 1$ . Now, if we assume that  $\Delta L$  is proportional to  $v_{DS}$ ,

$$\Delta L = \lambda' v_{DS}$$

where  $\lambda'$  is a process-technology parameter with the dimensions of  $\mu\text{m}/\text{V}$ , we obtain for  $i_D$ ,

$$i_D = \frac{1}{2} k'_n \frac{W}{L} \left( 1 + \frac{\lambda'}{L} v_{DS} \right) (v_{GS} - V_t)^2$$

Usually,  $\lambda'/L$  is denoted  $\lambda$ ,

$$\lambda = \frac{\lambda'}{L}$$



It follows that  $\lambda$  is a process-technology parameter with the dimensions of  $V^{-1}$  and that, for a given process,  $\lambda$  is inversely proportional to the length selected for the channel. In terms of  $\lambda$ , the expression for  $i_D$  becomes

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS}) \quad (4.22)$$

A typical set of  $i_D$ - $v_{DS}$  characteristics showing the effect of channel-length modulation is displayed in Fig. 4.16. The observed linear dependence of  $i_D$  on  $v_{DS}$  in the saturation region is represented in Eq. (4.22) by the factor  $(1 + \lambda v_{DS})$ . From Fig. 4.16 we observe that when the straight-line  $i_D$ - $v_{DS}$  characteristics are extrapolated they intercept the  $v_{DS}$ -axis at the point  $v_{DS} = -V_A$ , where  $V_A$  is a positive voltage. Equation (4.22), however, indicates that  $i_D = 0$



at  $v_{DS} = -1/\lambda$ . It follows that

$$V_A = \frac{1}{\lambda}$$

and thus  $V_A$  is a process-technology parameter with the dimensions of V. For a given process,  $V_A$  is proportional to the channel length  $L$  that the designer selects for a MOSFET. Just as in the case of  $\lambda$ , we can isolate the dependence of  $V_A$  on  $L$  by expressing it as

$$V_A = V'_A L$$

where  $V'_A$  is entirely process-technology dependent with the dimensions of V/ $\mu\text{m}$ . Typically,  $V'_A$  falls in the range of 5 V/ $\mu\text{m}$  to 50 V/ $\mu\text{m}$ . The voltage  $V_A$  is usually referred to as the Early voltage, after J.M. Early, who discovered a similar phenomenon for the BJT (Chapter 5).

resistance  $r_o$  as<sup>3</sup>

$$r_o \equiv \left[ \frac{\partial i_D}{\partial v_{DS}} \right]_{v_{GS} \text{ constant}}^{-1} \quad (4.23)$$

and using Eq. (4.22) results in

$$r_o = \left[ \lambda \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_t)^2 \right]^{-1} \quad (4.24)$$

which can be written as


$$r_o = \frac{1}{\lambda I_D} \quad (4.25)$$

or, equivalently,

$$r_o = \frac{V_A}{I_D} \quad (4.26)$$


where  $I_D$  is the drain current *without* channel-length modulation taken into account; that is,

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2$$

 

 **FIGURE 4.16** Effect of  $v_{DS}$  on  $i_D$  in the saturation region. The MOSFET parameter  $V_A$  depends on the process technology and, for a given process, is proportional to the channel length  $L$ .


 


 

**FIGURE 4.17** Large-signal equivalent circuit model of the  $n$ -channel MOSFET in saturation, incorporating the output resistance  $r_o$ . The output resistance models the linear dependence of  $i_D$  on  $v_{DS}$  and is given by Eq. (4.22).



**FIG 4.18 (A) SHOWS THE CIRCUIT SYMBOL FOR THE P-CHANNEL ENHANCEMENT TYPE MOSFET.(B) MODIFIED SYMBOL WITH AN ARROWHEAD ON THE SOURCE LEAD. (C) SIMPLIFIED CIRCUIT SYMBOL FOR THE CASE WHERE THE SOURCE IS CONNECTED TO THE BODY . (D) THE MOSFET WITH VOLTAGES APPLIED AND THE DIRECTIONS OF THE CURRENT FLOW INDICATED. NOTE THAT  $v_{GS}$  AND  $v_{DS}$  ARE NEGATIVE AND  $i_D$  FLOWS OUT OF THE DRAIN TERMINAL.**





or, equivalently,

$$v_{SG} \geq |V_t|$$

and apply a drain voltage that is more negative than the source voltage (i.e.,  $v_{DS}$  is negative or, equivalently,  $v_{SD}$  is positive). The current  $i_D$  flows out of the drain terminal, as indicated in the figure. To operate in the triode region  $v_{DS}$  must satisfy

$$v_{DS} \geq v_{GS} - V_t \quad (\text{Continuous channel}) \quad (4.28)$$

that is, the drain voltage must be higher than the gate voltage by at least  $|V_t|$ . The current  $i_D$  is given by the same equation as for NMOS, Eq. (4.11), except for replacing  $k'_n$  with  $k'_p$ ,

$$i_D = k'_p \frac{W}{L} \left[ (v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \quad (4.29)$$

where  $v_{GS}$ ,  $V_t$ , and  $v_{DS}$  are negative and the transconductance parameter  $k'_p$  is given by

$$k'_p = \mu_p C_{ox} \quad (4.30)$$

where  $\mu_p$  is the mobility of holes in the induced  $p$  channel. Typically,  $\mu_p = 0.25$  to  $0.5\mu_n$  and is process-technology dependent.

To operate in saturation,  $v_{DS}$  must satisfy the relationship

$$v_{DS} \leq v_{GS} - V_t \quad (\text{Pinched-off channel}) \quad (4.31)$$



that is, the drain voltage must be lower than (gate voltage +  $|V_t|$ ). The current  $i_D$  is given by the same equation used for NMOS, Eq. (4.22), again with  $k'_n$  replaced with  $k'_p$ ,


$$i_D = \frac{1}{2} k'_p \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS}) \quad (4.32)$$

where  $v_{GS}$ ,  $V_t$ ,  $\lambda$ , and  $v_{DS}$  are all negative. We should note, however, that in evaluating  $r_o$  using Eqs. (4.24) through (4.26), the magnitudes of  $\lambda$  and  $V_A$  should be used.

To recap, to turn a PMOS transistor on, the gate voltage has to be made lower than that of the source by at least  $|V_t|$ . To operate in the triode region, the drain voltage has to exceed that of the gate by at least  $|V_t|$ ; otherwise, the PMOS operates in saturation.



**FIG 4.19 SHOWS THE RELATIVE LEVELS OF THE TERMINAL VOLTAGES OF THE ENHANCEMENT TYPE PMOS TRANSISTOR FOR OPERATION IN THE TRIODE REGION AND IN THE SATURATION REGION.**

 

**4.4** An enhancement type NMOS transistor with  $V_t=0.7V$  has its source terminal grounded and a 1.5V dc applied to the gate. In what region does the device operate for

a)  $V_D=0.5V$  b)  $V_D=0.9V$  c)  $V_D=3V$

solution: The MOSFET operates in- triode region when  $V_{DS} < V_{OV}$  and in saturation region when  $V_{DS} > V_{OV}$

here  $V_{ov} = V_{GS} - V_t = 1.5 - 0.7 = 0.8V$

case a) when  $V_D = V_{DS} = 0.5V$  is applied

$$V_{DS} < V_{GS} - V_t$$

Device operates in triode region.

Case b) when  $V_{DS} = 0.9V$

$$V_{DS} > V_{GS} - V_t$$

Device operates in saturation region.

Case c) when  $V_{DS} = 3V$

$$V_{DS} > V_{GS} - V_t$$


Device operates in saturation region.



# MOSFET CIRCUITS AT DC

## EXAMPLE 4.2

Design the circuit of Fig. 4.20 so that the transistor operates at  $I_D = 0.4$  mA and  $V_D = +0.5$  V. The NMOS transistor has  $V_t = 0.7$  V,  $\mu_n C_{ox} = 100$   $\mu\text{A}/\text{V}^2$ ,  $L = 1$   $\mu\text{m}$ , and  $W = 32$   $\mu\text{m}$ . Neglect the channel-length modulation effect (i.e., assume that  $\lambda = 0$ ).

 

**FIGURE 4.20** Circuit for Example 4.2.



# SOLUTION FOR EXAMPLE 4.2

## Solution

Since  $V_D = 0.5$  V is greater than  $V_G$ , this means the NMOS transistor is operating in the saturation region, and we use the saturation-region expression of  $i_D$  to determine the required value of  $V_{GS}$ ,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

Substituting  $V_{GS} - V_t = V_{OV}$ ,  $I_D = 0.4$  mA = 400  $\mu$ A,  $\mu_n C_{ox} = 100$   $\mu$ A/V<sup>2</sup>, and  $W/L = 32/1$  gives

$$400 = \frac{1}{2} \times 100 \times \frac{32}{1} V_{OV}^2$$

which results in

$$V_{OV} = 0.5$$

Thus,

$$V_{GS} = V_t + V_{OV} = 0.7 + 0.5 = 1.2$$

Referring to Fig. 4.20, we note that the gate is at ground potential. Thus the source must be at  $-1.2$  V, and the required value of  $R_S$  can be determined from

$$\begin{aligned} R_S &= \frac{V_S - V_{SS}}{I_D} \\ &= \frac{-1.2 - (-2.5)}{0.4} = 3.25 \text{ k}\Omega \end{aligned}$$


To establish a dc voltage of +0.5 V at the drain, we must select  $R_D$  as follows:

$$\begin{aligned} R_D &= \frac{V_{DD} - V_D}{I_D} \\ &= \frac{2.5 - 0.5}{0.4} = 5 \text{ k}\Omega \end{aligned}$$



## EXAMPLE 4.3

Design the circuit in Fig. 4.21 to obtain a current  $I_D$  of  $80\text{ }\mu\text{A}$ . Find the value required for  $R$ , and find the dc voltage  $V_D$ . Let the NMOS transistor have  $V_t = 0.6\text{ V}$ ,  $\mu_n C_{ox} = 200\text{ }\mu\text{A/V}^2$ ,  $L = 0.8\text{ }\mu\text{m}$ , and  $W = 4\text{ }\mu\text{m}$ . Neglect the channel-length modulation effect (i.e., assume  $\lambda = 0$ ).

 

**FIGURE 4.21** Circuit for Example 4.3.

# SOLUTION FOR EXAMPLE 4.3

## Solution

Because  $V_{DG} = 0$ ,  $V_D = V_G$  and the FET is operating in the saturation region. Thus,

$$\begin{aligned} I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 \\ &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{OV}^2 \end{aligned}$$

from which we obtain  $V_{OV}$  as

$$\begin{aligned} V_{OV} &= \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} \\ &= \sqrt{\frac{2 \times 80}{200 \times (4/0.8)}} = 0.4 \text{ V} \end{aligned}$$

Thus,

$$V_{GS} = V_t + V_{OV} = 0.6 + 0.4 = 1 \text{ V}$$

and the drain voltage will be

$$V_D = V_G = +1 \text{ V}$$


The required value for  $R$  can be found as follows:

$$\begin{aligned} R &= \frac{V_{DD} - V_D}{I_D} \\ &= \frac{3 - 1}{0.080} = 25 \text{ k}\Omega \end{aligned}$$



## EXAMPLE 4.4

Design the circuit in Fig. 4.22 to establish a drain voltage of 0.1 V. What is the effective resistance between drain and source at this operating point? Let  $V_t = 1$  V and  $k'_n(W/L) = 1$  mA/V<sup>2</sup>.

 

**FIGURE 4.22** Circuit for Example 4.4.

**Solution**

Since the drain voltage is lower than the gate voltage by 4.9 V and  $V_t = 1$  V, the MOSFET is operating in the triode region. Thus the current  $I_D$  is given by

$$I_D = k'_n \frac{W}{L} \left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\begin{aligned} I_D &= 1 \times \left[ (5 - 1) \times 0.1 - \frac{1}{2} \times 0.01 \right] \\ &= 0.395 \text{ mA} \end{aligned}$$

The required value for  $R_D$  can be found as follows:

$$\begin{aligned} R_D &= \frac{V_{DD} - V_D}{I_D} \\ &= \frac{5 - 0.1}{0.395} = 12.4 \text{ k}\Omega \end{aligned}$$

In a practical discrete-circuit design problem one selects the closest standard value available for, say, 5% resistors—in this case, 12 k $\Omega$ ; see Appendix G. Since the transistor is operating in the triode region with a small  $V_{DS}$ , the effective drain-to-source resistance can be determined as follows:

$$\begin{aligned} r_{DS} &= \frac{V_{DS}}{I_D} \\ &= \frac{0.1}{0.395} = 253 \text{ }\Omega \end{aligned}$$







# EXAMPLE 4.5

## EXAMPLE 4.5

Analyze the circuit shown in Fig. 4.23(a) to determine the voltages at all nodes and the currents through all branches. Let  $V_t = 1$  V and  $k'_n(W/L) = 1$  mA/V<sup>2</sup>. Neglect the channel-length modulation effect (i.e., assume  $\lambda = 0$ ).

  

**FIGURE 4.23** (a) Circuit for Example 4.5. (b) The circuit with some of the analysis details shown.

## SOLUTION FOR EXAMPLE 4.5

### Solution

Since the gate current is zero, the voltage at the gate is simply determined by the voltage divider formed by the two 10-M $\Omega$  resistors,

$$V_G = V_{DD} \frac{R_{G2}}{R_{G2} + R_{G1}} = 10 \times \frac{10}{10 + 10} = +5 \text{ V}$$

With this positive voltage at the gate, the NMOS transistor will be turned on. We do not know, however, whether the transistor will be operating in the saturation region or in the triode region. We shall assume saturation-region operation, solve the problem, and then check the validity of our assumption. Obviously, if our assumption turns out not to be valid, we will have to solve the problem again for triode-region operation.

Refer to Fig. 4.23(b). Since the voltage at the gate is 5 V and the voltage at the source is  $I_D \text{ (mA)} \times 6 \text{ (k}\Omega) = 6I_D$ , we have

$$V_{GS} = 5 - 6I_D$$

Thus  $I_D$  is given by

$$\begin{aligned} I_D &= \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 \\ &= \frac{1}{2} \times 1 \times (5 - 6I_D - 1)^2 \end{aligned}$$

which results in the following quadratic equation in  $I_D$ :

$$18I_D^2 - 25I_D + 8 = 0$$

This equation yields two values for  $I_D$ : 0.89 mA and 0.5 mA. The first value results in a source voltage of  $6 \times 0.89 = 5.34$ , which is greater than the gate voltage and does not make physical sense as it would imply that the NMOS transistor is cut off. Thus,


$$\begin{aligned} I_D &= 0.5 \text{ mA} \\ V_S &= 0.5 \times 6 = +3 \text{ V} \\ V_{GS} &= 5 - 3 = 2 \text{ V} \\ V_D &= 10 - 6 \times 0.5 = +7 \text{ V} \end{aligned}$$

Since  $V_D > V_G - V_t$ , the transistor is operating in saturation, as initially assumed.



## EXAMPLE 4.6

Design the circuit of Fig. 4.24 so that the transistor operates in saturation with  $I_D = 0.5 \text{ mA}$  and  $V_D = +3 \text{ V}$ . Let the enhancement-type PMOS transistor have  $V_t = -1 \text{ V}$  and  $k'_p(W/L) = 1 \text{ mA/V}^2$ . Assume  $\lambda = 0$ . What is the largest value that  $R_D$  can have while maintaining saturation-region operation?

 

**FIGURE 4.24** Circuit for Example 4.6.

# SOLUTION FOR EXAMPLE 4.6

## Solution

Since the MOSFET is to be in saturation, we can write

$$\begin{aligned} I_D &= \frac{1}{2} k'_p \frac{W}{L} (V_{GS} - V_t)^2 \\ &= \frac{1}{2} k'_p \frac{W}{L} V_{OV}^2 \end{aligned}$$

Substituting  $I_D = 0.5$  mA and  $k'_p W/L = 1$  mA/V<sup>2</sup> and recalling that for a PMOS transistor  $V_{OV}$  is negative, we obtain

$$V_{OV} = -1 \text{ V}$$

and

$$V_{GS} = V_t + V_{OV} = -1 - 1 = -2 \text{ V}$$

Since the source is at +5 V, the gate voltage must be set to +3 V. This can be achieved by the appropriate selection of the values of  $R_{G1}$  and  $R_{G2}$ . A possible selection is  $R_{G1} = 2$  M $\Omega$  and  $R_{G2} = 3$  M $\Omega$ .

The value of  $R_D$  can be found from

$$R_D = \frac{V_D}{I_D} = \frac{3}{0.5} = 6 \text{ k}\Omega$$

Saturation-mode operation will be maintained up to the point that  $V_D$  exceeds  $V_G$  by  $|V_t|$ ; that is, until


$$V_{D_{\max}} = 3 + 1 = 4 \text{ V}$$

This value of drain voltage is obtained with  $R_D$  given by
 
$$R_D = \frac{4}{0.5} = 8 \text{ k}\Omega$$

 


**FIG 4.26 (a) SHOWS THE BASIC STRUCTURE OF THE COMMON SOURCE AMPLIFIER. (b) SHOWS THE GRAPHICAL CONSTRUCTION TO DETERMINE THE TRANSFER CHARACTERISTIC OF THE AMPLIFIER IN (a).**





**FIG4.26 (c) SHOWS THE TRANSFER CHARACTERISTICS SHOWING OPERATION AS AN AMPLIFIER BIASED AT POINT  $Q$ .**



(c)

# LARGE-SIGNAL OPERATION-THE TRANSFER CHARACTERISTIC

$$v_O = v_{DS} = V_{DD} - R_D i_D$$

## 4.4.2 Graphical Derivation of the Transfer Characteristic

The operation of the common-source circuit is governed by the MOSFET's  $i_D$ - $v_{DS}$  characteristics and by the relationship between  $i_D$  and  $v_{DS}$  imposed by connecting the drain to the power supply  $V_{DD}$  via resistor  $R_D$ , namely

$$v_{DS} = V_{DD} - R_D i_D \quad (4.36)$$

or, equivalently,

$$i_D = \frac{V_{DD}}{R_D} - \frac{1}{R_D} v_{DS} \quad (4.37)$$

Figure 4.26(b) shows a sketch of the MOSFET's  $i_D$ - $v_{DS}$  characteristic curves superimposed on which is a straight line representing the  $i_D$ - $v_{DS}$  relationship of Eq. (4.37). Observe that the straight line intersects the  $v_{DS}$ -axis at  $V_{DD}$  [since from Eq. (4.36)  $v_{DS} = V_{DD}$  at  $i_D = 0$ ] and has a slope of  $-1/R_D$ . Since  $R_D$  is usually thought of as the **load resistor** of the amplifier (i.e., the resistor across which the amplifier provides its output voltage), the straight line in Fig. 4.26(b) is known as the **load line**.

The graphical construction of Fig. 4.26(b) can now be used to determine  $v_O$  (equal to  $v_{DS}$ ) for each given value of  $v_I$  ( $v_{GS} = v_I$ ). Specifically, for any given value of  $v_I$ , we locate the corresponding  $i_D$ - $v_{DS}$  curve and find  $v_O$  from the point of intersection of this curve with the load line.



The graphical construction of Fig. 4.26(b) can now be used to determine  $v_O$  (equal to  $v_{DS}$ ) for each given value of  $v_I$  ( $v_{GS} = v_I$ ). Specifically, for any given value of  $v_I$ , we locate the corresponding  $i_D$ - $v_{DS}$  curve and find  $v_O$  from the point of intersection of this curve with the load line.

Qualitatively, the circuit works as follows: Since  $v_{GS} = v_I$ , we see that for  $v_I < V_t$ , the transistor will be cut off,  $i_D$  will be zero, and  $v_O = v_{DS} = V_{DD}$ . Operation will be at the point labeled A. As  $v_I$  exceeds  $V_t$ , the transistor turns on,  $i_D$  increases, and  $v_O$  decreases. Since  $v_O$  will initially be high, the transistor will be operating in the saturation region. This corresponds to points along the segment of the load line from A to B. We have identified a particular point in this region of operation and labeled it Q. It is obtained for  $V_{GS} = V_{IQ}$  and has the coordinates  $V_{OQ} = V_{DSQ}$  and  $I_{DQ}$ .

Saturation-region operation continues until  $v_O$  decreases to the point that it is below  $v_I$  by  $V_t$  volts. At this point,  $v_{DS} = v_{GS} - V_t$  and the MOSFET enters its triode region of operation. This is indicated in Fig. 4.26(b) by point B, which is at the intersection of the load line and the broken-line curve that defines the boundary between the saturation and the triode regions. Point B is defined by

$$V_{OB} = V_{IB} - V_t$$

For  $v_I > V_{IB}$ , the transistor is driven deeper into the triode region. Note that because the characteristic curves in the triode region are bunched together, the output voltage decreases slowly towards zero. Here we have identified a particular operating point C obtained for  $v_I = V_{DD}$ . The corresponding output voltage  $V_{OC}$  will usually be very small. This point-by-point determination of the transfer characteristic results in the transfer curve shown in Fig. 4.26(c). Observe that we have delineated its three distinct segments, each corresponding to one of the three regions of operation of MOSFET  $Q_1$ . We have also labeled the critical points of the transfer curve in correspondence with the points in Fig. 4.26(b).



### 4.4.3 Operation as a Switch

When the MOSFET is used as a switch, it is operated at the extreme points of the transfer curve. Specifically, the device is turned off by keeping  $v_i < V_t$  resulting in operation somewhere on the segment XA with  $v_o = V_{DD}$ . The switch is turned on by applying a voltage close to  $V_{DD}$ , resulting in operation close to point C with  $v_o$  very small (at C,  $v_o = V_{OC}$ ). At this juncture we observe that the transfer curve of Fig. 4.26(c) is of the form presented in Section 1.7 for the digital logic inverter. Indeed, the common-source MOS circuit can be used as a logic inverter with the “low” voltage level close to 0 V and the “high” level close to  $V_{DD}$ . More elaborate MOS logic inverters are studied in Section 4.10.

### 4.4.4 Operation as a Linear Amplifier

To operate the MOSFET as an amplifier we make use of the saturation-mode segment of the transfer curve. The device is biased at a point located somewhere close to the middle of the curve; point Q is a good example of an appropriate bias point. The dc bias point is also called the **quiescent point**, which is the reason for labeling it Q. The voltage signal to be amplified  $v_i$  is then superimposed on the dc voltage  $V_{IQ}$  as shown in Fig. 4.26(c). By keeping  $v_i$  sufficiently small to restrict operation to an almost linear segment of the transfer curve, the resulting output voltage signal  $v_o$  will be proportional to  $v_i$ . That is, the amplifier will be very nearly linear, and  $v_o$  will have the same waveform as  $v_i$  except that it will be larger by a factor equal to the voltage gain of the amplifier at Q,  $A_v$ , where

$$A_v \equiv \left. \frac{dv_o}{dv_i} \right|_{v_i = V_{IQ}} \quad (4.38)$$

Thus the voltage gain is equal to the slope of the transfer curve at the bias point Q. Observe that the slope is negative, and thus the basic CS amplifier is inverting. This should be also evident from the waveforms of  $v_i$  and  $v_o$  shown in Fig. 4.26(c). It should be obvious that if the amplitude of the input signal  $v_i$  is increased, the output signal will become distorted since operation will no longer be restricted to an almost linear segment of the transfer curve.

We shall return to the small-signal operation of the MOSFET in Section 4.6. For the time being, however, we wish to make an important observation about selecting an appropriate location for the bias point Q. Since the output signal will be superimposed on the dc voltage at the drain  $V_{OQ}$  or  $V_{DSQ}$ , it is important that  $V_{DSQ}$  be of such value to allow for the required output signal swing. That is,  $V_{DSQ}$  should be lower than  $V_{DD}$  by a sufficient amount and higher than  $V_{OB}$  by a sufficient amount to allow for the required positive and negative output signal swing, respectively. If  $V_{DSQ}$  is too close to  $V_{DD}$ , the positive peaks of the output signals might “bump” into  $V_{DD}$  and would be clipped off, because the MOSFET would turn off for part of the cycle. We speak of this situation as the circuit not having sufficient “headroom.” Similarly, if  $V_{DSQ}$  is too close to the boundary of the triode region, the MOSFET would enter the triode region for the part of the cycle near the negative peaks, resulting in a distorted output signal. We speak of this situation as the circuit not having sufficient “legroom.” Finally, it is important to note that although we made our comments on the selection of bias-point location in the context of a given transfer curve, the circuit designer also has to decide on a value for  $R_D$ , which of course determines the transfer curve. It is therefore more appropriate when considering the location of the bias point Q to do so with reference to the  $i_D$ - $v_{DS}$  plane. This point is further illustrated by the sketch in Fig. 4.27.





## Analytical Expressions for the Transfer Characteristic

The  $i$ - $v$  relationships that describe the MOSFET operation in the three regions—cutoff, saturation, and triode—can be easily used to derive analytical expressions for the three segments of the transfer characteristic in Fig. 4.26(a).

**The Cutoff-Region Segment, XA** Here,  $v_I \leq V_t$ , and  $v_O = V_{DD}$ .

**The Saturation-Region Segment, AQB** Here,  $v_I \geq V_t$ , and  $v_O \geq v_I - V_t$ . Neglecting channel-length modulation and substituting for  $i_D$  from

$$i_D = \frac{1}{2}(\mu_n C_{ox})\left(\frac{W}{L}\right)(v_I - V_t)^2$$

into

$$v_O = V_{DD} - R_D i_D$$

gives

$$v_O = V_{DD} - \frac{1}{2}R_D\mu_n C_{ox}\frac{W}{L}(v_I - V_t)^2 \quad (4.39)$$

We can use this relationship to derive an expression for the incremental voltage gain  $A_v$  at a bias point Q at which  $v_I = V_{IQ}$  as follows:

$$A_v \equiv \left. \frac{dv_O}{dv_I} \right|_{v_I = V_{IQ}}$$



Thus,

$$A_v = -R_D \mu_n C_{ox} \frac{W}{L} (V_{I_Q} - V_t) \quad (4.40)$$

Observe that the voltage gain is proportional to the values of  $R_D$ , the transconductance parameter  $k'_n = \mu_n C_{ox}$ , the transistor aspect ratio  $W/L$ , and the overdrive voltage at the bias point  $V_{OV} = V_{I_Q} - V_t$ .

Another simple and very useful expression for the voltage gain can be obtained by substituting  $v_i = V_{I_Q}$  and  $v_o = V_{O_Q}$  in Eq. (4.39), utilizing Eq. (4.40), and substituting  $V_{I_Q} - V_t = V_{OV}$ . The result is

$$A_v = -\frac{2(V_{DD} - V_{O_Q})}{V_{OV}} = -\frac{2V_{RD}}{V_{OV}} \quad (4.41)$$

where  $V_{RD}$  is the dc voltage across the drain resistor  $R_D$ ; that is,  $V_{RD} = V_{DD} - V_{O_Q}$ .

The end point of the saturation-region segment is characterized by

$$V_{OB} = V_{IB} - V_t \quad (4.42)$$

**The Triode-Region Segment, BC** Here,  $v_I \geq V_t$ , and  $v_O \leq v_I - V_t$ . Substituting for  $i_D$  by the triode-region expression

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[ (v_I - V_t) v_O - \frac{1}{2} v_O^2 \right]$$

into

$$v_O = V_{DD} - R_D i_D$$

gives

$$v_O = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} \left[ (v_I - V_t) v_O - \frac{1}{2} v_O^2 \right]$$

The portion of this segment for which  $v_O$  is small is given approximately by

$$v_O \cong V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} (v_I - V_t) v_O$$

which reduces to

$$v_O = V_{DD} / \left[ 1 + R_D \mu_n C_{ox} \frac{W}{L} (v_I - V_t) \right] \quad (4.43)$$

We can use the expression for  $r_{DS}$ , the drain-to-source resistance near the origin of the  $i_D$ - $v_{DS}$  plane (Eq. 4.13),

$$r_{DS} = 1 / \left[ \mu_n C_{ox} \frac{W}{L} (v_I - V_t) \right]$$



together with Eq. (4.43) to obtain

$$v_O = V_{DD} \frac{r_{DS}}{r_{DS} + R_D} \quad (4.44)$$

which makes intuitive sense: For small  $v_O$ , the MOSFET operates as a resistance  $r_{DS}$  (whose value is determined by  $v_I$ ), which forms with  $R_D$  a voltage divider across  $V_{DD}$ . Usually,  $r_{DS} \ll R_D$ , and Eq. (4.44) reduces to

$$v_O \cong V_{DD} \frac{r_{DS}}{R_D} \quad (4.45)$$

## BIASING IN MOS AMPLIFIER CIRCUITS

An appropriate dc operating point or bias point is characterized by a stable and predictable dc drain current  $I_D$  and by a dc drain-to-source voltage  $V_{DS}$  that ensures operation in the saturation region for all expected input-signal levels

Biasing by Fixing  $V_{GS}$



FIG 4.27 SHOWS THE TWO LOAD LINES AND CORRESPONDING BIAS POINTS. BIAS POINT  $Q_1$  DOES NOT LEAVE SUFFICIENT ROOM FOR POSITIVE SIGNAL SWING AT THE DRAIN (TOO CLOSE TO  $V_{DD}$ ). BIAS POINT  $Q_2$  IS TOO CLOSE TO THE BOUNDARY OF THE TRIODE REGION AND MIGHT NOT ALLOW FOR SUFFICIENT NEGATIVE SIGNAL SWING.

 


FIG 4.29 SHOWS THE USE OF FIXED BIAS (CONSTANT  $V_{GS}$ ) CAN RESULT IN A LARGE VARIABILITY IN THE VALUE OF  $I_D$ . DEVICES 1 AND 2 REPRESENT EXTREMES AMONG UNITS OF THE SAME TYPE.


 


 

FIG 4.30 SHOWS BIASING USING A FIXED VOLTAGE AT THE GATE,  $V_G$ , AND A RESISTANCE IN THE SOURCE LEAD,  $R_S$ , (a) BASIC ARRANGEMENT; (b) REDUCED VARIABILITY IN  $I_D$ ;




An excellent biasing technique for discrete MOSFET circuits consists of fixing the dc voltage at the gate,  $V_G$ , and connecting a resistance in the source lead, as shown in Fig. 4.30(a). For this circuit we can write

$$V_G = V_{GS} + R_S I_D \quad (4.46)$$


Now, if  $V_G$  is much greater than  $V_{GS}$ ,  $I_D$  will be mostly determined by the values of  $V_G$  and  $R_S$ . However, even if  $V_G$  is not much larger than  $V_{GS}$ , resistor  $R_S$  provides *negative feedback*, which acts to stabilize the value of the bias current  $I_D$ . To see how this comes about consider the case when  $I_D$  increases for whatever reason. Equation (4.46) indicates that since  $V_G$  is constant,  $V_{GS}$  will have to decrease. This in turn results in a decrease in  $I_D$ , a change that is opposite to that initially assumed. Thus the action of  $R_S$  works to keep  $I_D$  as constant as possible. This negative feedback action of  $R_S$  gives it the name **degeneration resistance**, a name that we will appreciate much better at a later point in this text.

Figure 4.30(b) provides a graphical illustration of the effectiveness of this biasing scheme. Here we show the  $i_D$ - $v_{GS}$  characteristics for two devices that represent the extremes of a batch of MOSFETs. Superimposed on the device characteristics is a straight line that represents the constraint imposed by the bias circuit—namely, Eq. (4.46). The intersection of this straight line with the  $i_D$ - $v_{GS}$  characteristic curve provides the coordinates ( $I_D$  and  $V_{GS}$ ) of the bias point. Observe that compared to the case of fixed  $V_{GS}$ , here the variability obtained in  $I_D$  is much smaller. Also, note that the variability decreases as  $V_G$  and  $R_S$  are made larger (providing a bias line that is less steep).


FIG 4.30 SHOWS BIASING USING A FIXED VOLTAGE AT THE GATE,  $V_G$ , AND A RESISTANCE IN THE SOURCE LEAD,  $R_S$ , (c) PRACTICAL IMPLEMENTATION USING A SINGLE SUPPLY; (d) COUPLING OF A SIGNAL SOURCE TO THE GATE USING A CAPACITOR  $C_{C1}$ ; (e) PRACTICAL IMPLEMENTATION USING TWO SUPPLIES.

 

(c)

 


(d)

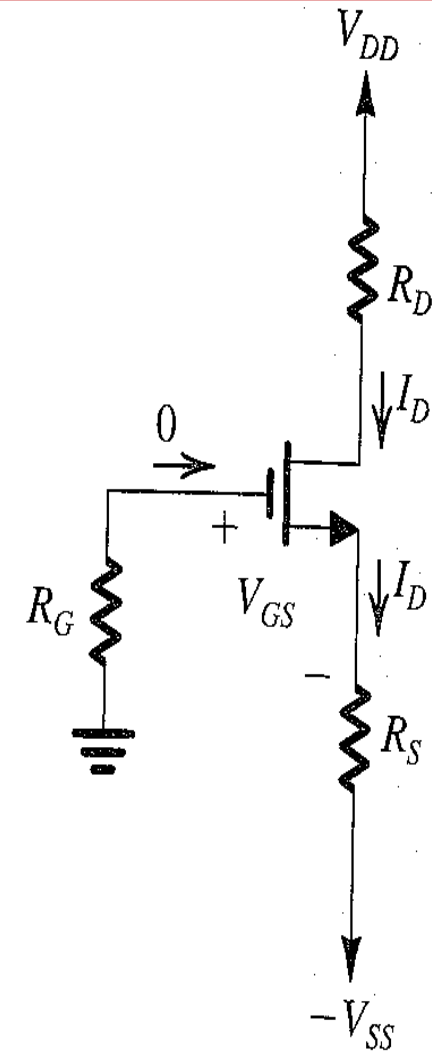

(e)

FIG 4.32 SHOWS THE BIASING OF THE MOSFET USING A LARGE DRAIN TO GATE FEEDBACK RESISTOR  $R_G$ .

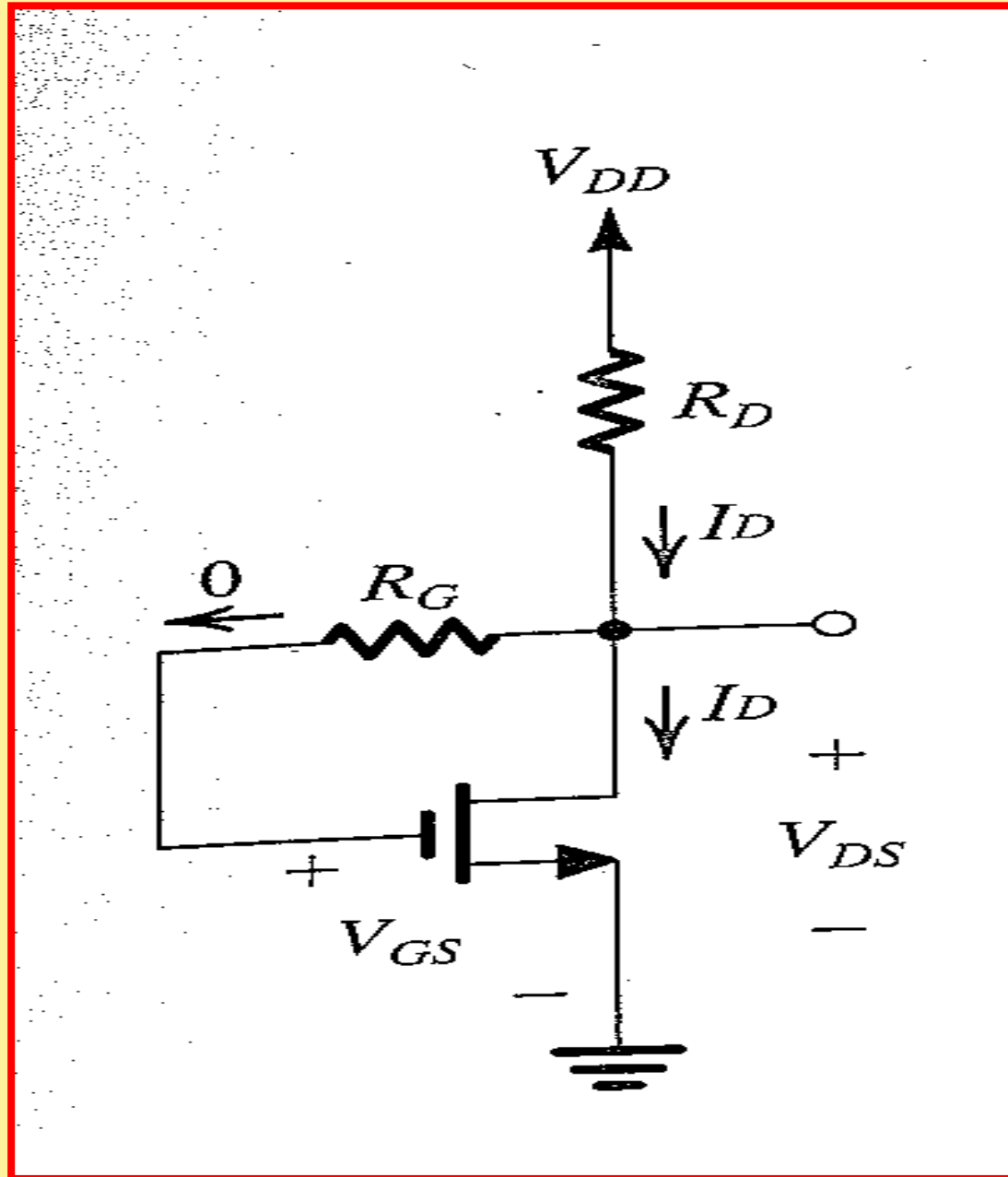

$$V_{GS} = V_{DS} = V_{DD} - R_D I_D$$


$$V_{DD} = V_{GS} + R_D I_D$$

Thus the negative feedback or degeneration provided by  $R_G$  works to keep the value of  $I_D$  as constant as possible.


can be utilized as a CS amplifier by applying the input voltage signal to the gate via a coupling capacitor so as not to disturb the dc bias conditions already established. The amplified output signal at the drain can be coupled to another part of the circuit, again via a capacitor. We shall consider such a CS amplifier circuit in Section 4.6. There we will learn that this circuit has the drawback of a rather limited output voltage signal swing.



FIG 4.33(a) SHOWS THE BIASING THE MOSFET USING A CONSTANT-CURRENT SOURCE  $I$ .(b) IMPLEMENTATION OF THE CONSTANT-CURRENT SOURCE  $I$  USING A CURRENT MIRROR.

 

(a)

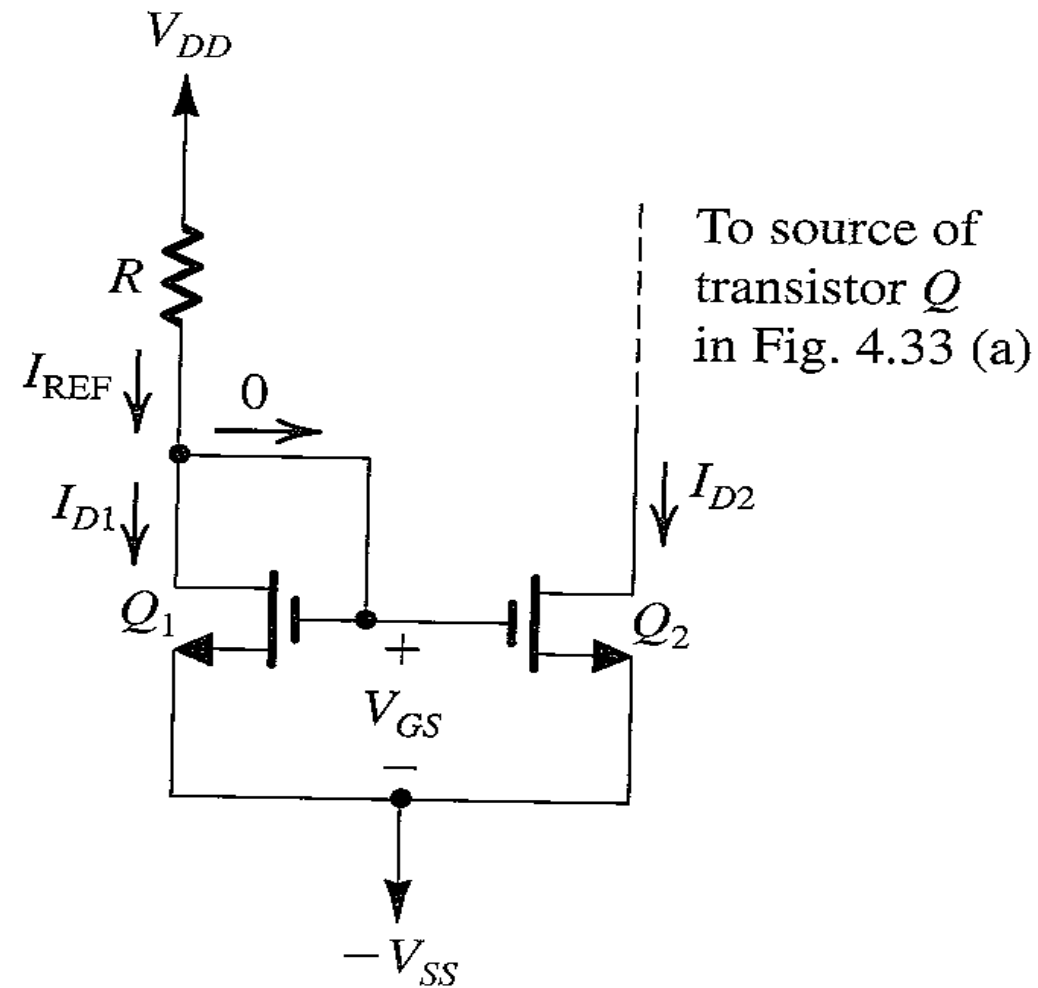

(b)



The most effective scheme for biasing a MOSFET amplifier is that using a constant-current source. Figure 4.33(a) shows such an arrangement applied to a discrete MOSFET. Here  $R_G$  (usually in the  $M\Omega$  range) establishes a dc ground at the gate and presents a large resistance to an input signal source that can be capacitively coupled to the gate. Resistor  $R_D$  establishes an appropriate dc voltage at the drain to allow for the required output signal swing while ensuring that the transistor always remains in the saturation region.

A circuit for implementing the constant-current source  $I$  is shown in Fig. 4.33(b). The heart of the circuit is transistor  $Q_1$ , whose drain is shorted to its gate and thus is operating in the saturation region, such that

$$I_{D1} = \frac{1}{2}k'_n \left(\frac{W}{L}\right)_1 (V_{GS} - V_t)^2 \quad (4.50)$$

where we have neglected channel-length modulation (i.e., assumed  $\lambda = 0$ ). The drain current of  $Q_1$  is supplied by  $V_{DD}$  through resistor  $R$ . Since the gate currents are zero,

$$I_{D1} = I_{REF} = \frac{V_{DD} + V_{SS} - V_{GS}}{R} \quad (4.51)$$



where the current through  $R$  is considered to be the *reference current* of the current source and is denoted  $I_{\text{REF}}$ . Given the parameter values of  $Q_1$  and a desired value for  $I_{\text{REF}}$ , Eqs. (4.50) and (4.51) can be used to determine the value of  $R$ . Now consider transistor  $Q_2$ ; It has the same  $V_{GS}$  as  $Q_1$ ; thus if we assume that it is operating in saturation, its drain current, which is the desired current  $I$  of the current source, will be

$$I = I_{D2} = \frac{1}{2}k'_n \left(\frac{W}{L}\right)_2 (V_{GS} - V_t)^2 \quad (4.52)$$

where we have neglected channel-length modulation. Equations (4.51) and (4.52) enable us to relate the current  $I$  to the reference current  $I_{\text{REF}}$ ,

$$I = I_{\text{REF}} \frac{(W/L)_2}{(W/L)_1} \quad (4.53)$$

Thus  $I$  is related to  $I_{\text{REF}}$  by the ratio of the aspect ratios of  $Q_1$  and  $Q_2$ . This circuit, known as a **current mirror**, is very popular in the design of IC MOS amplifiers and will be studied in great detail in Chapter 6.

