
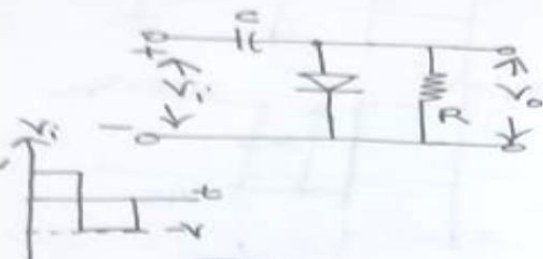


①

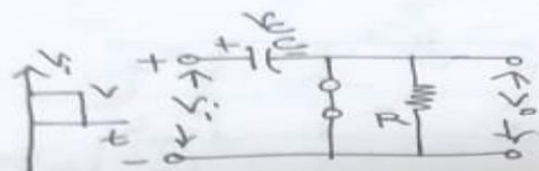

Ideal

During +ve half of applied i/p




Apply KVL to i/p loop,

$$v_i - v_c = 0$$

$$v_c = v_i = V$$

$$v_o = 0V$$

During -ve half of i/p

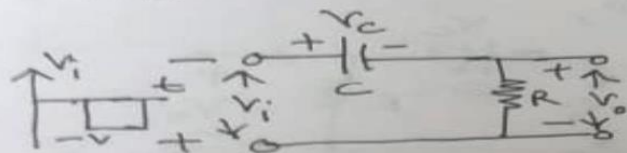


Apply KVL to CKT,

$$-v_i - v_c - v_o = 0$$



$$v_o = -v_i - v_c$$

$$v_o = -V - V = -2V$$

Clamper v_i (Ideal)

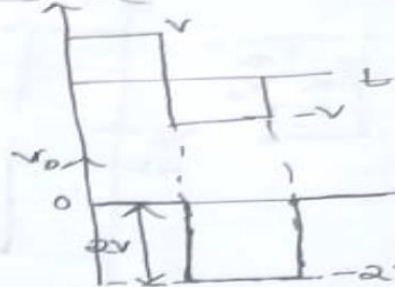

Practical

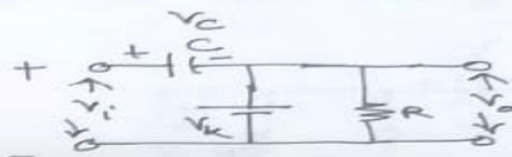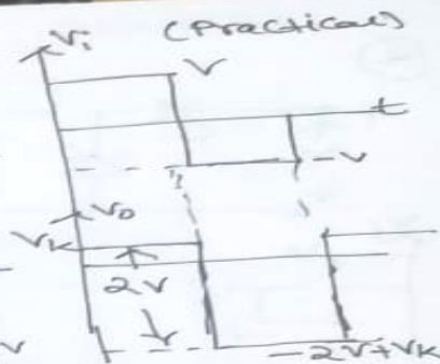


Apply KVL to i/p loop

$$v_i - v_c - v_k = 0$$

$$v_c = v_i - v_k$$

$$v_c = V - v_k$$

$$v_o = v_k$$

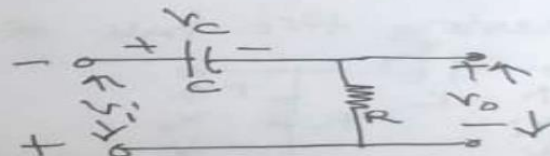


$$-v_i - v_c - v_o = 0$$

$$v_o = -v_i - (v_i - v_k)$$


$$v_o = -2V + V_k$$

②


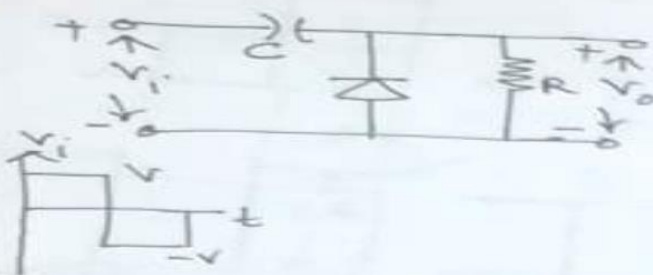


Ideal

During the half of applied v_i

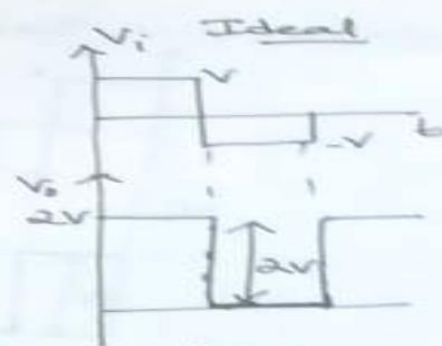

Practical

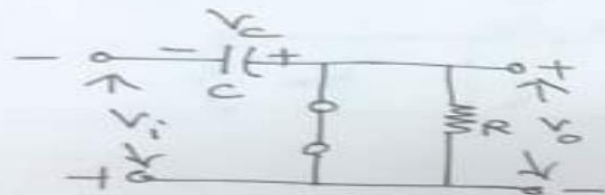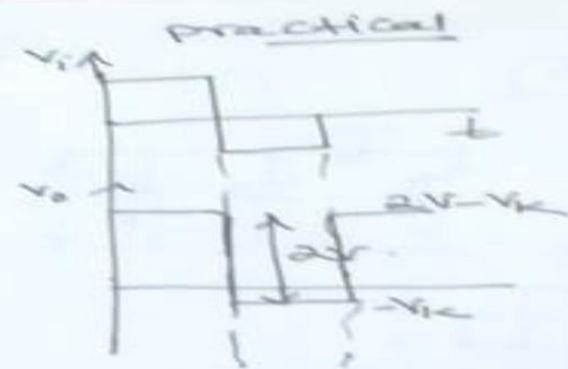


apply KVL to i_p loop,

$$-V_i + V_C = 0$$

$$V_C = V_i = V$$

$$V_o = 0$$

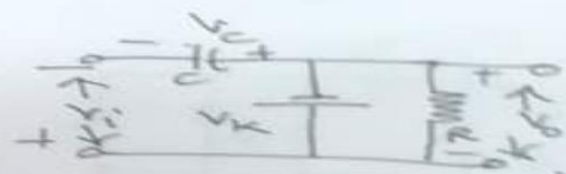

apply KVL to i_p loop


$$-V_i + V_C + V_r = 0$$

$$V_C = V_i - V_r$$

$$V_C = V - V_r$$

$$V_o = V_r = -V_r$$


During the half of applied v_i ,

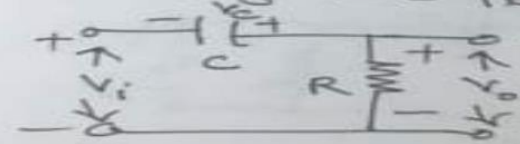

$$V_i + V_C = V_o$$

$$V + V = V_o$$

$$2V = V_o$$

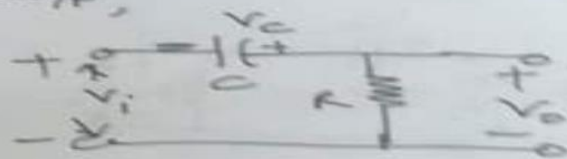


$$V_i + V_C = V_o$$

$$V_o = V_i + V - V_r$$


$$= V + V - V_r = 2V - V_r$$

3

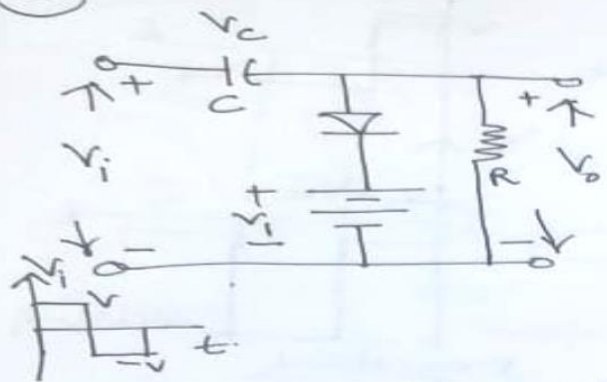

During +ve half.

Ideal

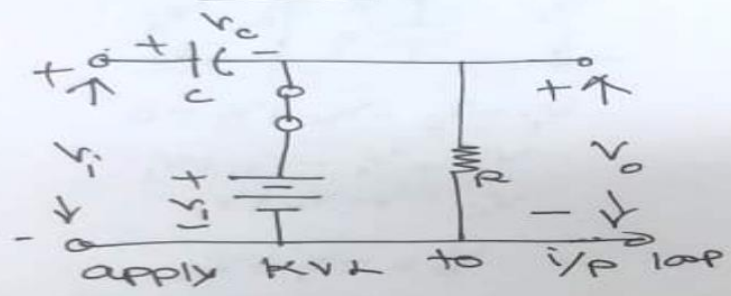

apply KVL to i/p loop

$$V_i - V_c - V_i = 0$$


$$V_c = V_i - V_i$$

$$V_c = V - V_i$$

apply KVL to o/p loop


$$V_i - V_o = 0, V_o = V_i$$

During -ve half.

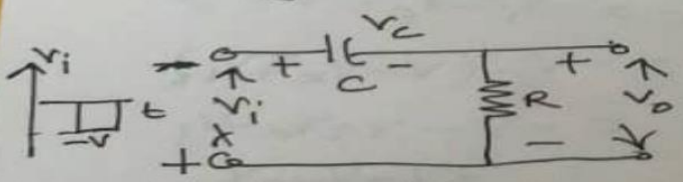


$$-V_i - V_c - V_o = 0$$
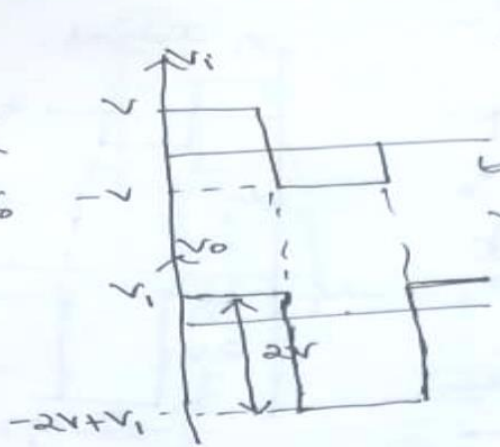
$$V_o = -V_i - V_c = -V - V + V_i = -2V + V_i$$



Practical

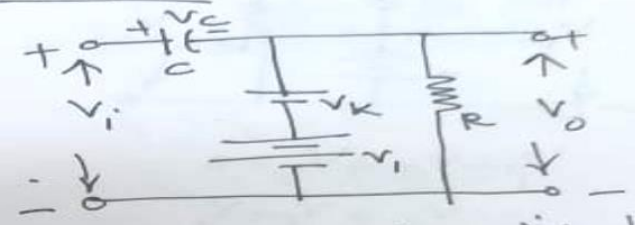

apply KVL to i/p loop


$$V_i - V_c - V_c - V_i = 0$$

$$V_c = V_i - V_c - V_i$$

$$V_c = V - V_c - V_i$$

$$V_o = V_i + V_c$$

During -ve half.

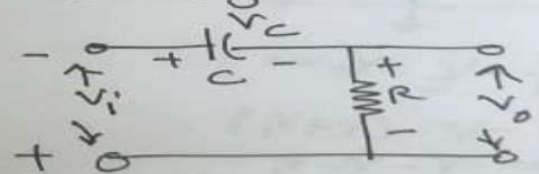


$$-V_i - V_c - V_o = 0$$


$$V_o = -V_i - (V - V_c - V_i)$$

$$= -V - V + V_c + V_i$$


$$= -2V + V_c + V_i$$

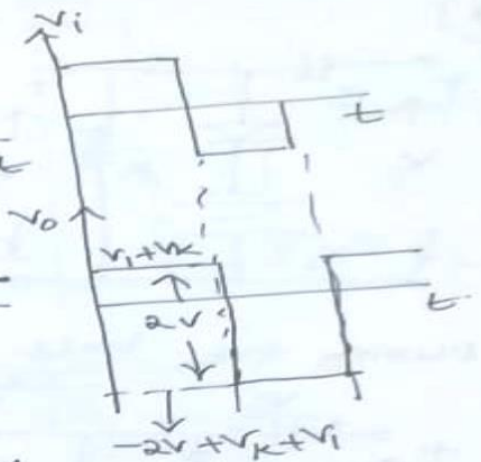

4

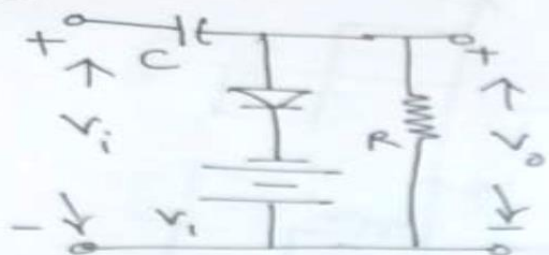

During the half Ideal

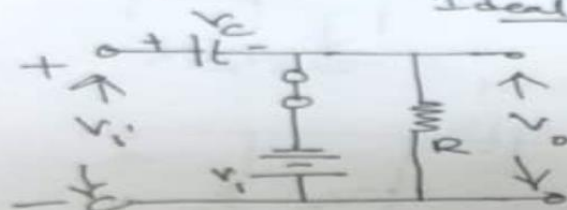


$$v_i - v_c + v_i = 0$$

$$v_c = v_i + v_i$$

$$v_c = v + v_i$$

$$v_o = -v_i$$

During -ve half,



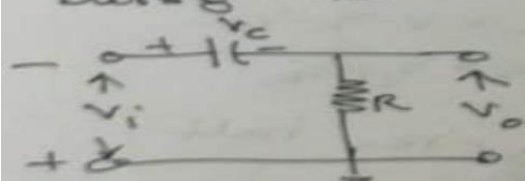


$$-v_i - v_c - v_o = 0$$

$$v_o = -v - (v + v_i)$$

$$= -v - v - v_i$$

$$= -2v - v_i$$

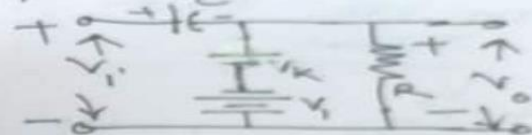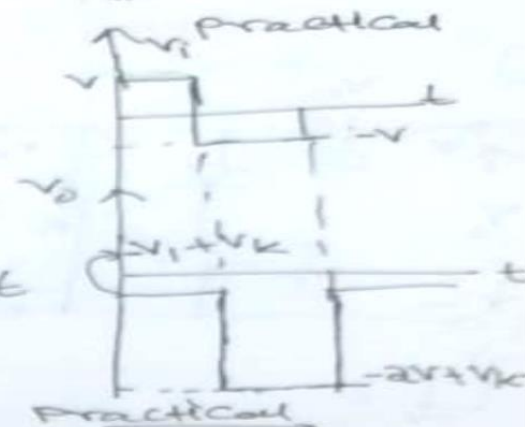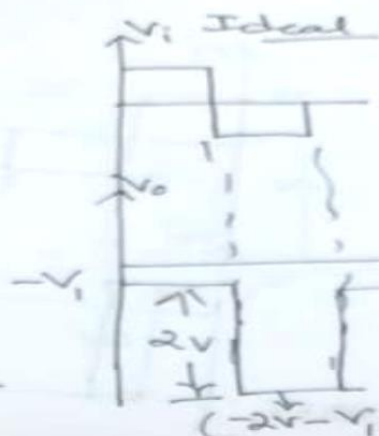


$$v_i - v_c - v_k + v_i = 0$$

$$v_c = v_i - v_k + v_i$$

$$v_c = v - v_k + v_i$$

$$v_o = -v_i + v_k$$

During -ve half

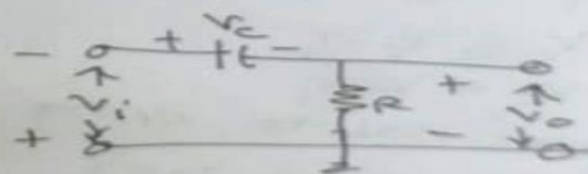

$$-v_i - v_c - v_o = 0$$


$$v_o = -v_i - v_c$$

$$= -v - (v - v_k + v_i)$$


$$= -v - v + v_k - v_i$$

$$= -2v + v_k - v_i$$

5

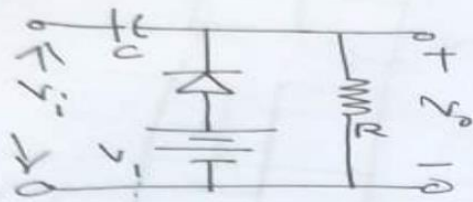

During $-ve$ half cycle

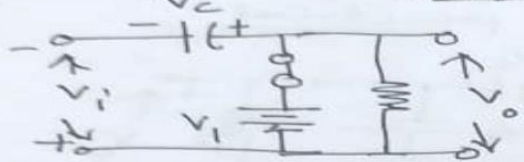


$$-V_i + V_C - V_1 = 0$$

$$V_C = V_i + V_1$$

$$V_C = V + V_1$$

$$V_o = V_i$$



During $+ve$ half cycle

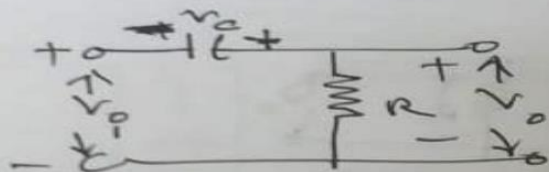


$$V_o = V_i + V_C$$

$$V_o = V + (V + V_1)$$

$$= 2V + V_1$$

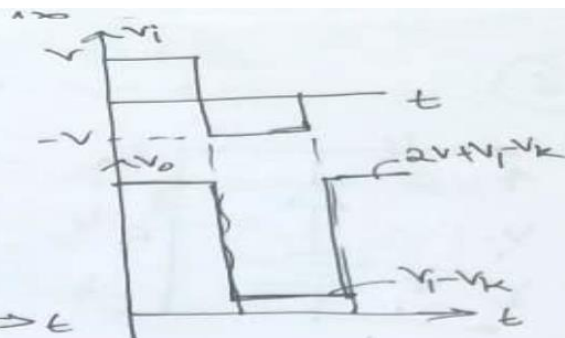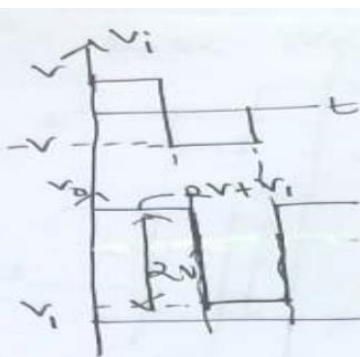

practical

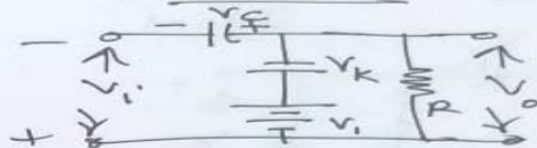


$$-V_i + V_C + V_K - V_1 = 0$$

$$V_C = V_i - V_K + V_1$$

$$V_C = V - V_K + V_1$$

$$V_o = V_i - V_K$$

During $+ve$ half cycle

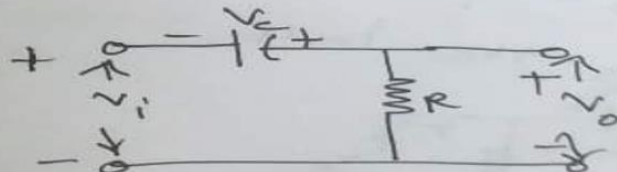

$$V_i + V_C - V_o = 0$$




$$V_o = V_i + V_C$$

$$V_o = V + (V - V_K + V_1)$$


$$V_o = V + V - V_K + V_1$$

$$V_o = 2V + V_1 - V_K$$

6

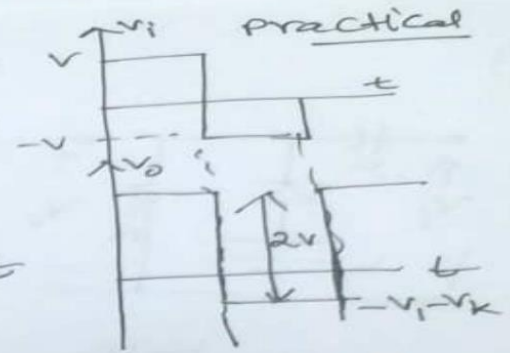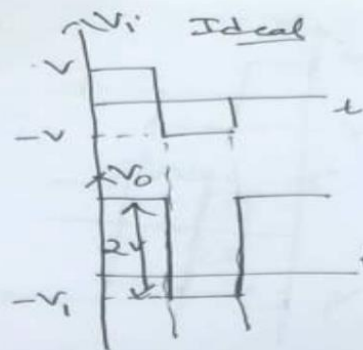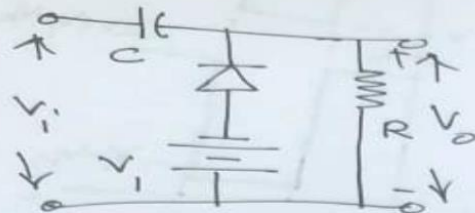

During $-v_c$ half
Ideal

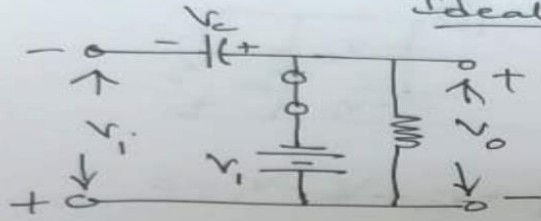


$$-v_i + v_c + V = 0$$

$$v_c = v_i - V$$

$$v_c = V - v_i$$

$$v_o = -v_i$$

During $+v_c$ half.

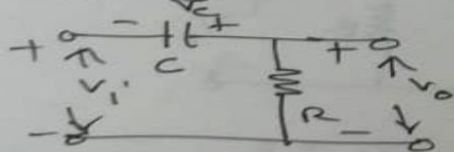

$$v_i + v_c - v_o = 0$$


$$v_o = v_i + v_c$$

$$= V + (V - v_i)$$

$$= V + V - v_i$$

$$= 2V - v_i$$

During $-v_c$ half
practical

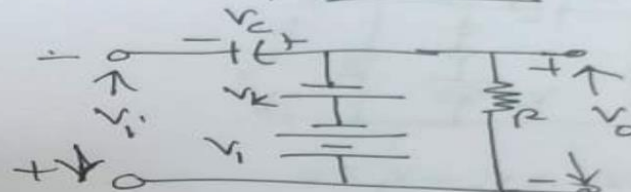


$$-v_i + v_c + V_K + V = 0$$

$$v_c = v_i - V_K - V$$

$$v_c = V - V_K - v_i$$

$$v_o = -v_i - V_K$$

During $+v_c$ half.

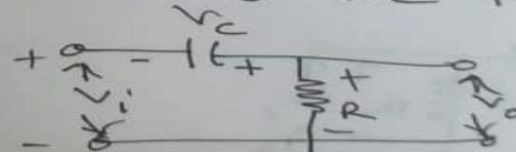




$$v_i + v_c - v_o = 0$$

$$v_o = v_i + v_c$$

$$= V + (V - V_K - v_i)$$

$$= 2V - V_K - v_i$$


Determine v_o for the network of Fig.

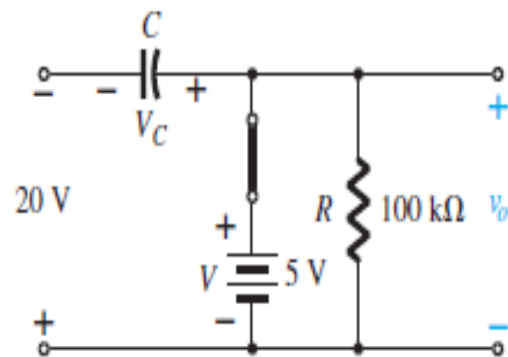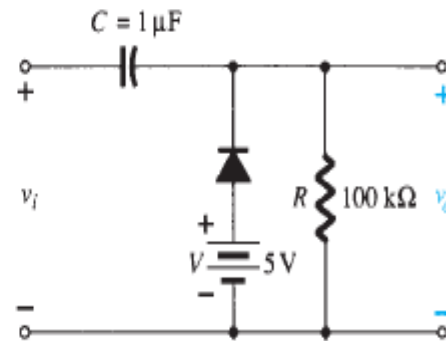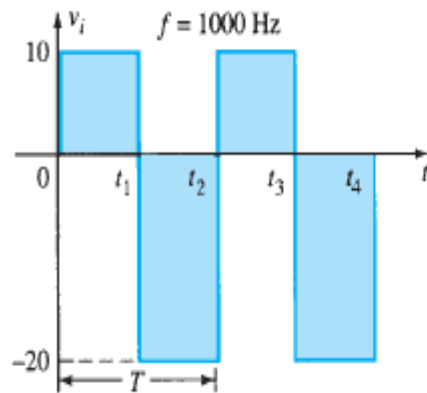

$$-20 \text{ V} + V_C - 5 \text{ V} = 0$$



$$V_C = 25 \text{ V}$$

$$v_o = 5 \text{ V}$$

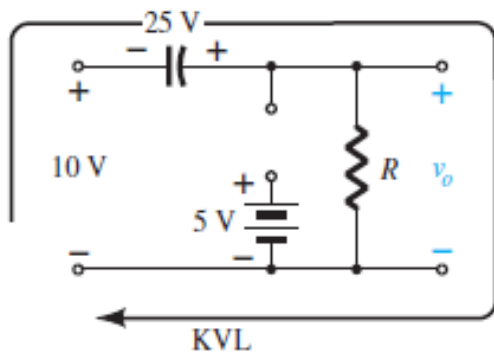

$$+10\text{ V} + 25\text{ V} - v_o = 0$$


$$v_o = 35\text{ V}$$

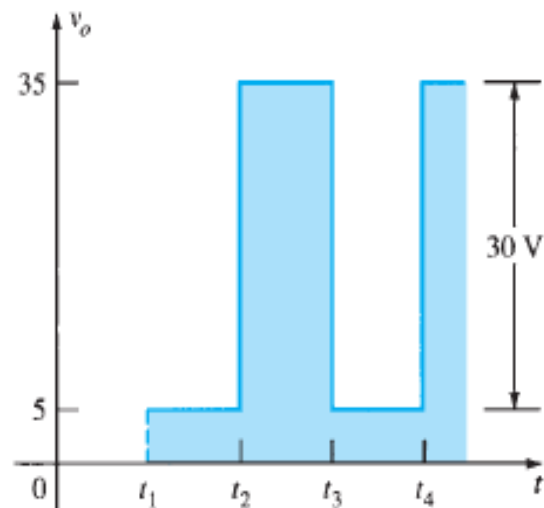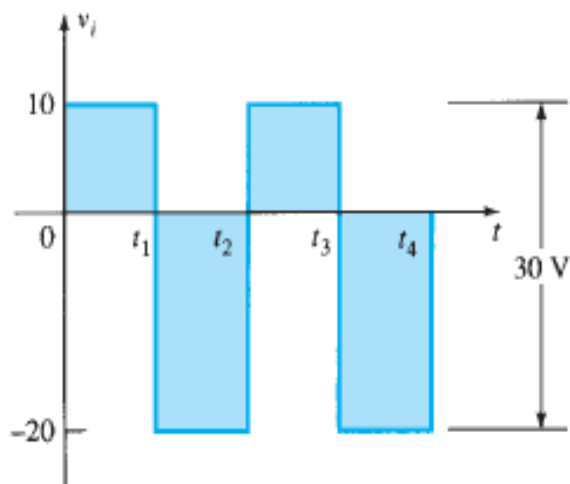

using a silicon diode with $V_K = 0.7 \text{ V}$.

$$+5 \text{ V} - 0.7 \text{ V} - v_o = 0$$
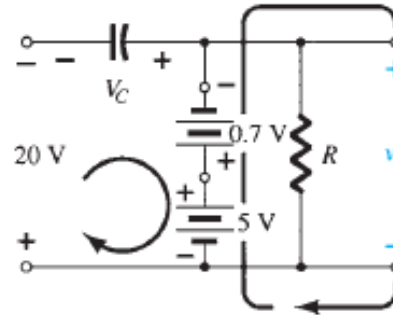
$$v_o = 5 \text{ V} - 0.7 \text{ V} = 4.3 \text{ V}$$



1 Kirchhoff's voltage law results in

$$-20 \text{ V} + V_C + 0.7 \text{ V} - 5 \text{ V} = 0$$

$$V_C = 25 \text{ V} - 0.7 \text{ V} = 24.3 \text{ V}$$

$$+10 \text{ V} + 24.3 \text{ V} - v_o = 0$$

$$v_o = 34.3 \text{ V}$$

